

# Hardware Design and Lab

## Lab\_5 Group Report

Name: 林奕為

Vending Machine

## Contents

Vending Machine .....	3
How do I design the module: .....	3
State Diagram:.....	5
Block Diagram: .....	6

# Vending Machine

## How do I design the module:

This design employs the concept of Finite State Machine, the vending machine has 7 states, and they are INSERT, INSERT\_MAX, IS\_COFFEE, IS\_COKE, IS\_OOLONG, IS\_WATER, CANCEL respectively, the current money which is denoted by total\_money will be displayed using 7\_segment LED light.

The one\_second\_decrement submodule handle the decrement of the total\_money, the input value will be decremented by \$5 each second using a counter counting to 1M times under the 1Mhz clk signal generated by BASYS3 FPGA board.

The definition of states:

### INSERT:

The initial state, only during this state can the user insert money into the machine, and at any time the state will enter INSERT if rst\_n signal is triggered.

After examining the current total\_money, if the total\_money is greater than the price of the beverage (coffee = \$80, coke = \$30, oolong = \$25, water = \$20), the corresponding LED will be turn on, and if the key on the keyboard belong to that beverage is press down, it will enter next state depending on the item the user bought.

If total\_money  $\geq$  \$100, enter state INSERT\_MAX.

### INSERT\_MAX:

Under this state, the user cannot insert money anymore, but the user can still buy the beverages.

### IS\_COFFEE:

If the a key on the keyboard is press down and the total\_money  $\geq$  \$80, enter this state, then the total\_money will become total\_money - \$80 instantly, and in each second afterward, total\_money will be decremented by \$5 until it becomes \$0 by means of one\_second\_decrement module, and eventually enter INSERT state again.

### IS\_COKE:

Like IS\_COFFEE, but the price is \$30, and the corresponding key on the keyboard is s.

IS\_OOLONG:

Similar to IS\_COFFEE, but the price is \$25, and the corresponding key on the keyboard is s.


IS\_WATER:

Similar to IS\_COFFEE, but the price is \$20, and the corresponding key on the keyboard is s.

CANCEL:


Upon hitting btn\_down on the FPGA the state will become CANCEL, and the total\_money will be decremented by \$5 each second until \$0, eventually enter INSERT state again.

## State Diagram:

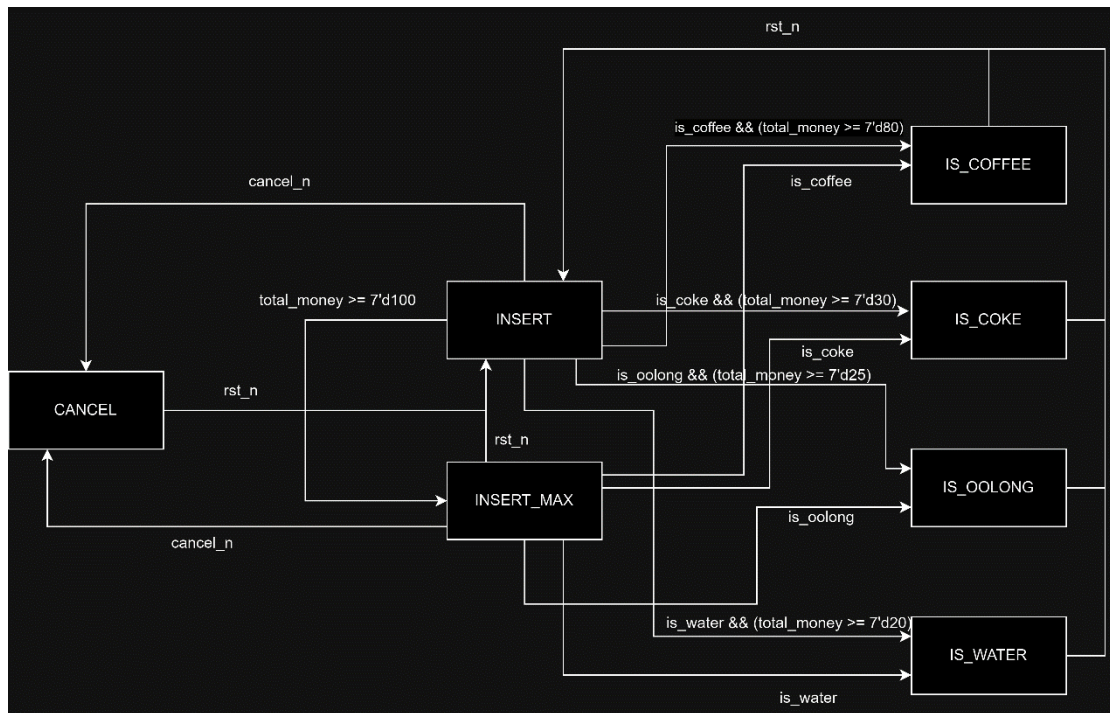


## Block Diagram:


Global\_schematic:

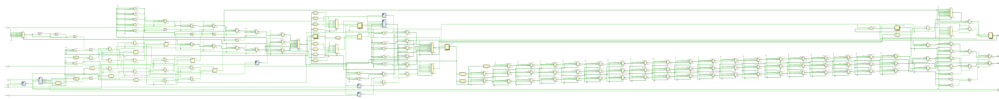

One\_second\_decrement:

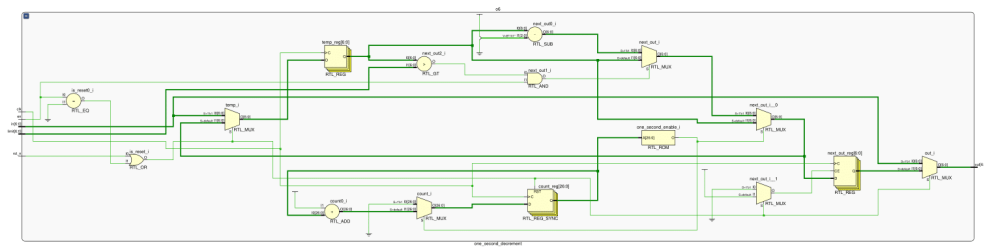


One\_signal:

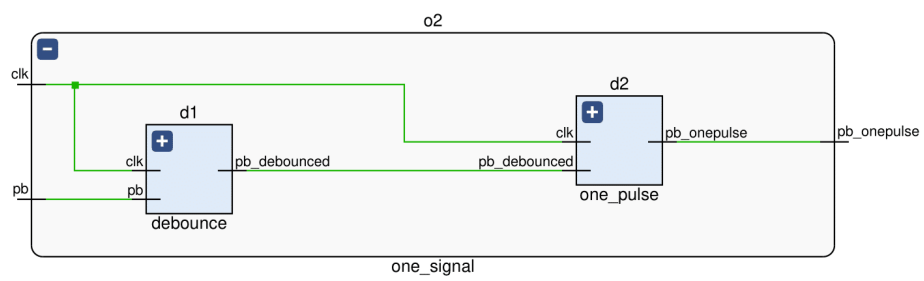



Debounce:

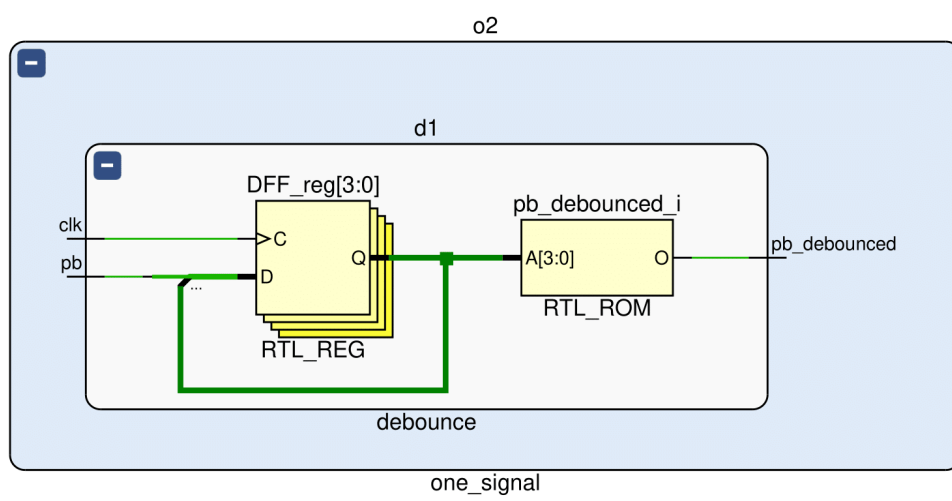

One\_pulse:

